

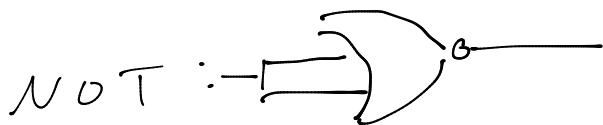


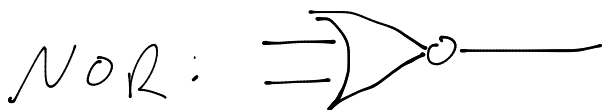1 NOR is a complete base 3.1
given NAND is complete.



NAND:

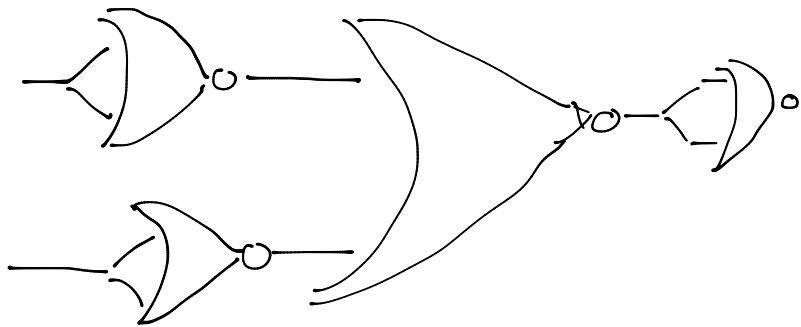

NAND is complete,

so NOR is also

complete because we

can transform it into NAND.